

The Computation of Winding Impedances in a Three-Winding Transformer

W. H. Kersting

February 2014

Transformer data:

$$\text{kVA}_p := 15000$$

$$\text{kVLL}_p := 69$$

$$\text{kVA}_s := 10000$$

$$\text{kVLL}_s := 13.2$$

$$\text{kVA}_t := 5000$$

$$\text{kVLL}_t := 2.4$$

where: p = primary winding

s = secondary winding

t = tertiary winding

Transfer impedance measurements in per-cent:

$$Z\%_{ps} := 0.15 + j \cdot 7 \quad \text{per-cent based upon 15,000 kVA}$$

$$Z\%_{pt} := 0.2 + j \cdot 9 \quad \text{per-cent based upon 15,000 kVA}$$

$$Z\%_{st} := 0.17 + j \cdot 8 \quad \text{per-cent based upon 10,000 kVA}$$

Convert $Z_{pu_{st}}$ to per-cent based upon 15,000 kVA

$$Z\%_{st} := Z\%_{st} \cdot \frac{\text{kVA}_p}{\text{kVA}_s} \quad Z\%_{st} = 0.255 + j \cdot 12$$

Convert transfer impedances to per-unit

$$Z_{pu_{ps}} := \frac{Z\%_{ps}}{100} \quad Z_{pu_{ps}} = 0.0015 + j \cdot 0.07$$

$$Z_{pu_{pt}} := \frac{Z\%_{pt}}{100} \quad Z_{pu_{pt}} = 0.002 + j \cdot 0.09$$

$$Z_{pu_{st}} := \frac{Z\%_{st}}{100} \quad Z_{pu_{st}} = 0.00255 + j \cdot 0.12$$

Calculate winding impedances in per-unit

$$Z_{pu_p} := \frac{1}{2} \cdot (Z_{pu_{ps}} + Z_{pu_{pt}} - Z_{pu_{st}}) \quad Z_{pu_p} = 0.0005 + j \cdot 0.02$$

$$Z_{pu_s} := \frac{1}{2} \cdot (Z_{pu_{ps}} + Z_{pu_{st}} - Z_{pu_{pt}}) \quad Z_{pu_s} = 0.001 + j \cdot 0.05$$

$$Z_{pu_t} := \frac{1}{2} \cdot (Z_{pu_{pt}} + Z_{pu_{st}} - Z_{pu_{ps}}) \quad Z_{pu_t} = 0.0015 + j \cdot 0.07$$

Compute base impedance for each winding using primary kVA as common base:

$$\text{kVA}_{\text{base}} := \text{kVA}_p$$

$$\text{kVA}_{\text{base}} = 15000$$

$$\text{Primary bases:} \quad \text{kVLN}_p := \frac{\text{kVLL}_p}{\sqrt{3}} \quad \text{kVLN}_p = 39.8372$$

$$\text{Ibase}_p := \frac{\text{kVA}_{\text{base}}}{\sqrt{3} \cdot \text{kVLL}_p} \quad \text{Ibase}_p = 125.5109$$

$$\text{Zbase}_p := \frac{\text{kVLN}_p \cdot 1000}{\text{Ibase}_p} \quad \text{Zbase}_p = 317.4$$

$$\text{Secondary bases:} \quad \text{kVLN}_s := \frac{\text{kVLL}_s}{\sqrt{3}} \quad \text{kVLN}_s = 7.621$$

$$\text{Ibase}_s := \frac{\text{kVA}_{\text{base}}}{\sqrt{3} \cdot \text{kVLL}_s} \quad \text{Ibase}_s = 656.0799$$

$$\text{Zbase}_s := \frac{\text{kVLN}_s \cdot 1000}{\text{Ibase}_s} \quad \text{Ibase}_s = 656.0799$$

$$\text{Tertiary delta bases:} \quad \text{Ibase}_t := \frac{\text{kVA}_{\text{base}}}{3 \cdot \text{kVLL}_t} \quad \text{Ibase}_t = 2083.3333$$

$$\text{Zbase}_t := \frac{\text{kVLL}_t \cdot 1000}{\text{Ibase}_t} \quad \text{Zbase}_t = 1.152$$

Note: The base tertiary impedance is used to compute the actual tertiary winding impedance in Ohms inside the delta.

Compute the winding impedances in Ohms:

$$Z_p := Z_{pu_p} \cdot \text{Zbase}_p \quad Z_p = 0.1508 + j \cdot 6.348j$$

$$Z_s := Z_{pu_s} \cdot \text{Zbase}_s \quad Z_s = 0.0119 + j \cdot 0.5808j$$

$$Z_t := Z_{pu_t} \cdot \text{Zbase}_t \quad Z_t = 0.0018 + j \cdot 0.0806j$$